

# Lecture # 8

Introduction to Sequential Circuits/Synchronous versus Asynchronous/Latches/Flip-Flops/Characteristic Tables and Equations

By: Muhammad Zain Uddin

email: [zuddin@iba.edu.pk](mailto:zuddin@iba.edu.pk)



# Digital Logic Design

Muhammad Zain Uddin

Lecturer,  
IBA

# Combinational versus Sequential

---

Two classes of digital circuits


- Combinational Circuits
- Sequential Circuits

Combinational Circuit

- $\text{Outputs} = F(\text{Inputs})$
- Function of Inputs only
- NO internal memory

Sequential Circuit

 - Outputs is a function of Inputs and internal Memory
- There is an internal memory that stores the state of the circuit
- Time is very important: memory changes with time



# Introduction to Sequential Circuits

A Sequential circuit consists of:

1. Memory elements:

- Latches or Flip-Flops
- Store the **Present State**


2. Combinational Logic

- Computes the **Outputs** of the circuit

Outputs depend on Inputs and Current State

- Computes the **Next State** of the circuit

 Next State also depends on the Inputs and the Present State



# Two Types of Sequential Circuits

---

## 1. **Synchronous** Sequential Circuit

- Uses a clock signal as an additional input
- Changes in the memory elements are controlled by the clock
- Changes happen at discrete instances of time

## 2. **Asynchronous** Sequential Circuit


- No clock signal
- Changes in the memory elements can happen at any instance of time

Our focus will be on Synchronous Sequential Circuits

- Easier to design and analyze than asynchronous sequential circuits

# Synchronous Sequential Circuits

---

 

Synchronous sequential circuits use a **clock signal**


The clock signal is an input to the memory elements

The clock determines **when** the memory should be updated

The **present state** = output value of memory (stored)

The **next state** = input value to memory (not stored yet)

# The Clock

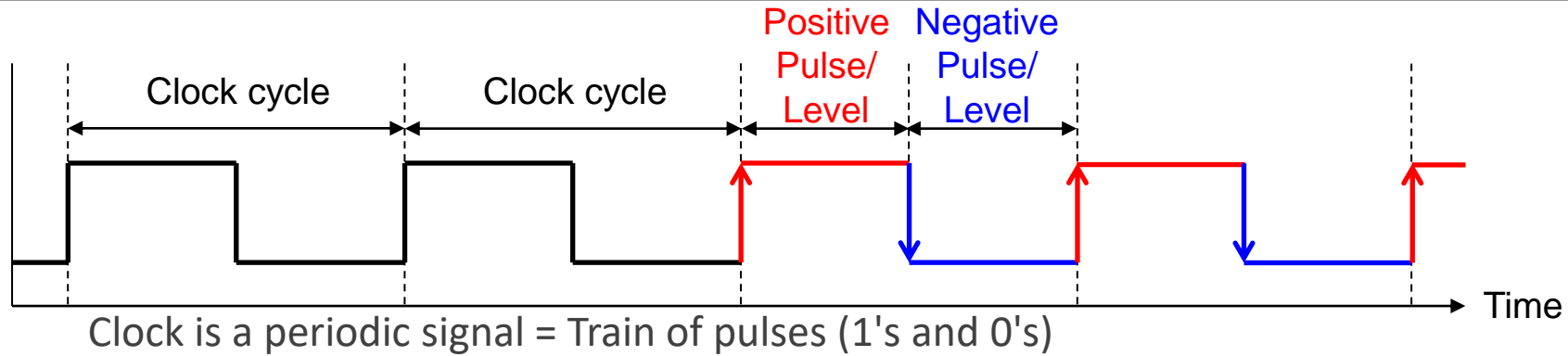

The same clock cycle repeats indefinitely over time

**Positive Pulse:** when the **level** of the clock is **1**

**Negative Pulse:** when the **level** of the clock is **0**

**Rising Edge:** when the clock goes **from 0 to 1**

**Falling Edge:** when the clock goes **from 1 down to 0**

# Memory Elements

---

Memory can store and maintain binary state (0's or 1's)

- Until directed by an input signal to change state

Main difference between memory elements

- Number of inputs they have
- How the inputs affect the binary state

Two main types:

- Latches are level-sensitive (the level of the clock)
- Flip-Flops are edge-sensitive (sensitive to the edge of the clock)

Flip-Flops are used in synchronous sequential circuits

Flip-Flops are built with latches




# SR Latch

A **latch** is a memory element that can store 0 or 1

An **SR Latch** can be built using two **cross-coupled** NOR gates

Two inputs:  $S$  (Set) and  $R$  (Reset)

Two outputs:  $Q$  and  $\bar{Q}$

 


(a) Logic diagram

S	R	Q	$\bar{Q}$	
1	0	1	0	Set state
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined


(b) Function table

# SR Latch Operation

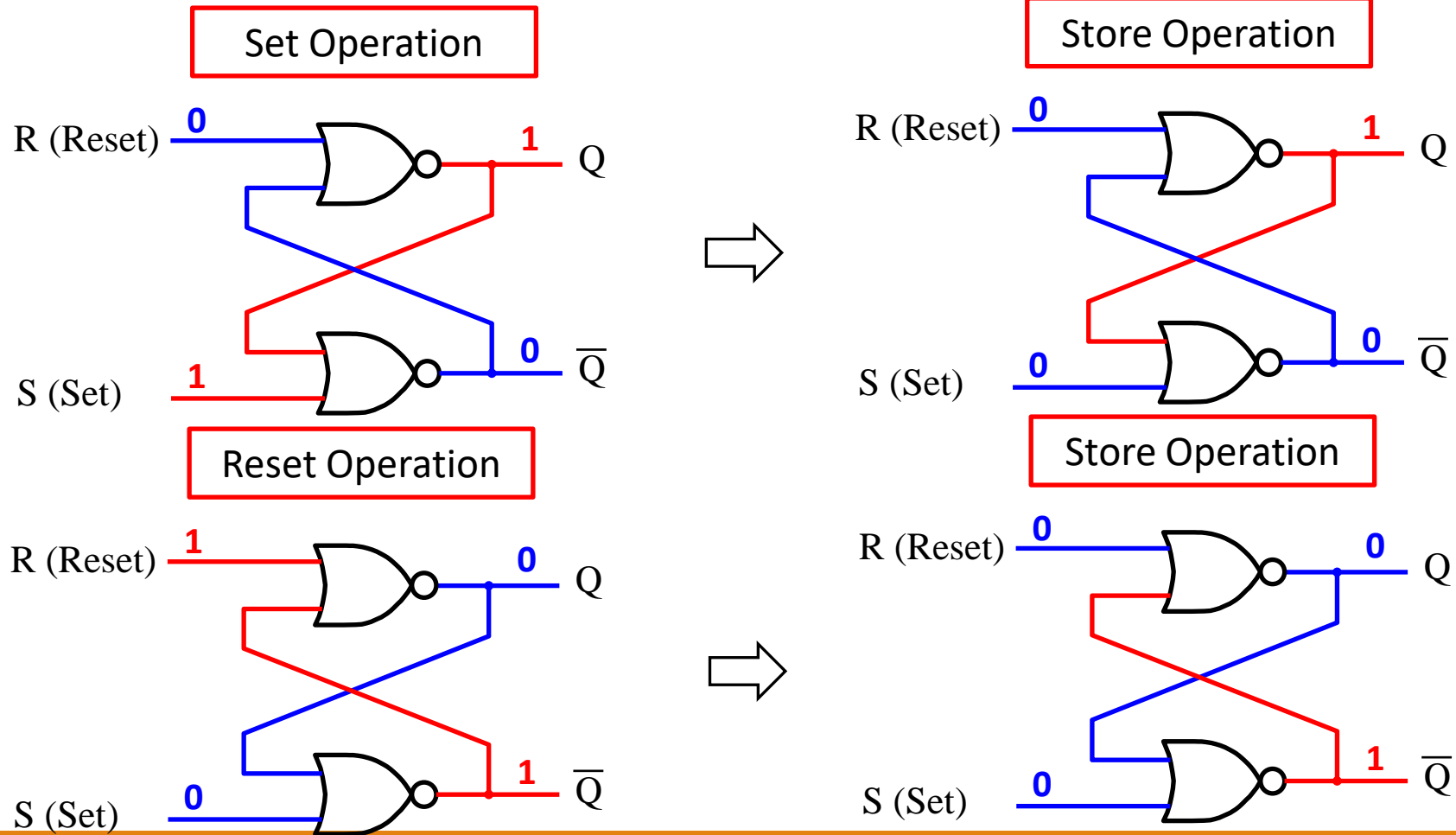

# SR Latch Invalid Operation

Invalid Operation

 


$S = R = 1$  should never be used


If S and R change from  $1 \rightarrow 0$  simultaneously then race condition (oscillation) occurs

Final Q and  $\bar{Q}$  are unknown



Race Condition

 


Unknown State

 

# Timing Diagram of an SR Latch

 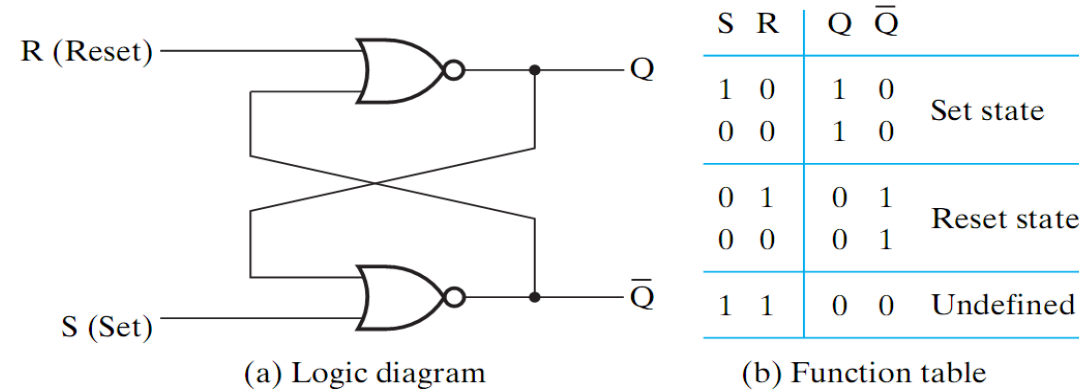


# Gated SR Latch with Clock Enable

 

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; Set state
1	1	1	Undefined

- ❖ An additional Clock (enable) input signal **C** is used
- ❖ Clock controls **when** the state of the latch can be changed
- ❖ When **C=0**, the S and R inputs have no effect on the latch  
The latch will remain in the same state, regardless of S and R
- ❖ When **C=1**, then normal SR latch operation

# S R Latch with NAND Gates

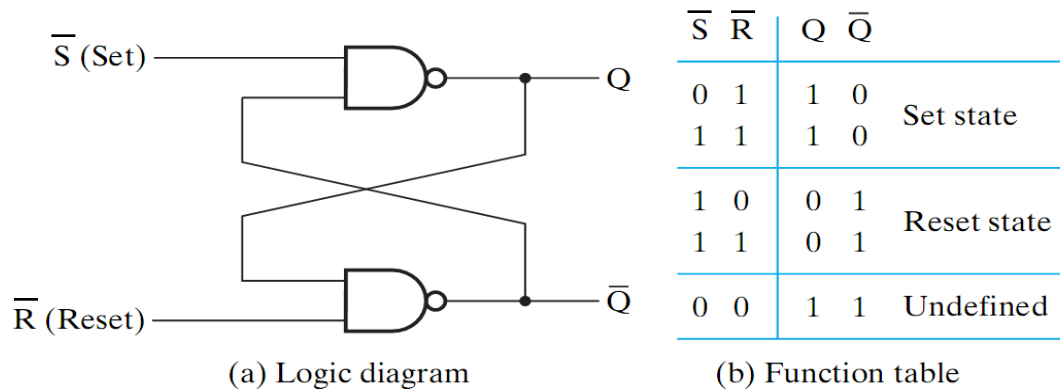

Known as  
the  $\bar{S} \bar{R}$  Latch

If  $\bar{S} = 0$  and  $\bar{R} = 1$  then **Set** ( $Q = 1$ ,  $\bar{Q} = 0$ )






If  $\bar{S} = 1$  and  $\bar{R} = 0$  then **Reset** ( $Q = 0$ ,  $\bar{Q} = 1$ )

When  $\bar{S} = \bar{R} = 1$ ,  $Q$  and  $\bar{Q}$  are unchanged (remain the same)

The latch stores its outputs  $Q$  and  $\bar{Q}$  as long as  $\bar{S} = \bar{R} = 1$


When  $\bar{S} = \bar{R} = 0$ ,  $Q$  and  $\bar{Q}$  are undefined (should never be used)

# S R Latch Operation

 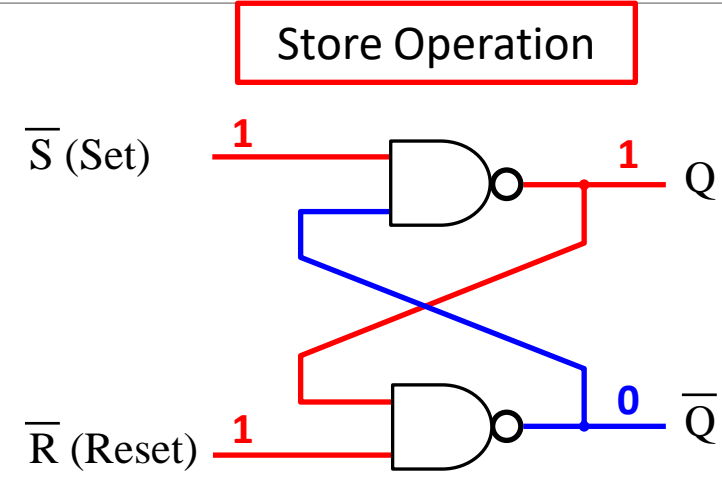 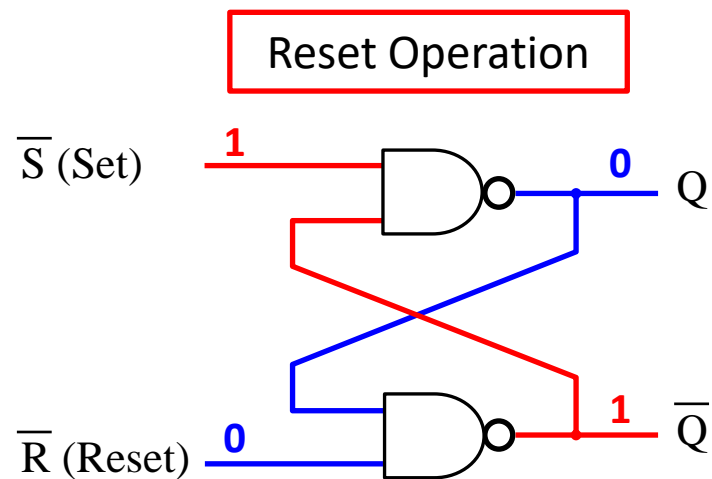 

# S R Latch Invalid Operation

Invalid Operation

 


$\overline{S} = \overline{R} = 0$  should never be used

If  $\overline{S}$  and  $\overline{R}$  change from  $0 \rightarrow 1$  simultaneously then race condition (oscillation) occurs


Final Q and  $\overline{Q}$  are unknown



Race Condition

 


Unknown State

 



# Gated SR Latch with Clock Enable

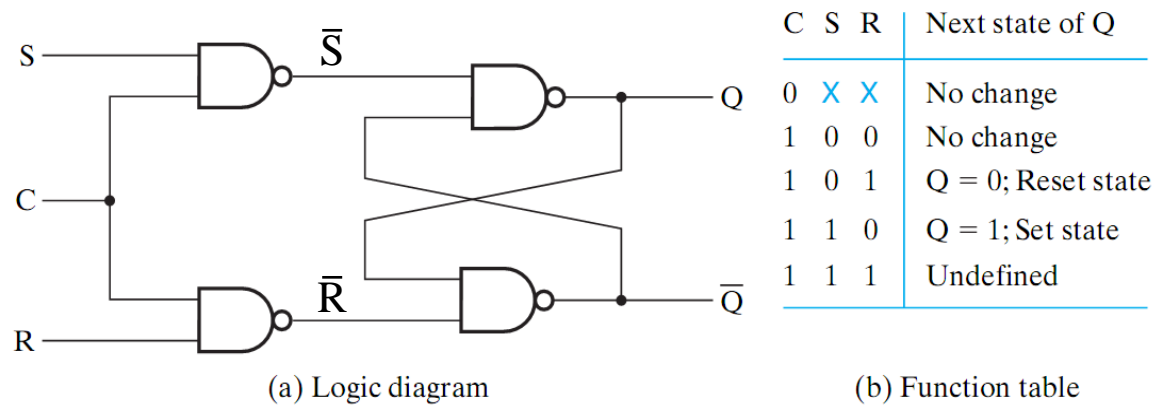

An additional Clock (enable) input signal **C** is used


Clock controls **when** the state of the latch can be changed

When **C=0**, the latch remains in the same state

When **C=1**, then normal latch operation

The NAND gates invert the **S** and **R** inputs when **C=1**

# D-Latch with Clock Enable

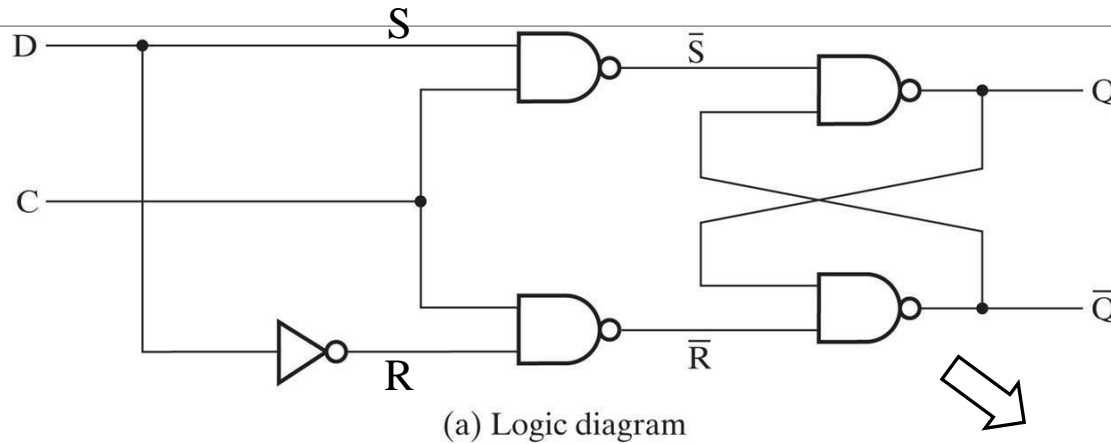

C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

(b) Function table


One data input  $D$

$S = D$  and  $R = \bar{D}$



No undefined state

Inverter can be removed

When  $C = 1$ ,  $R = \bar{S} = \bar{D}$

 


# Timing of a D-Latch with Clock Enable

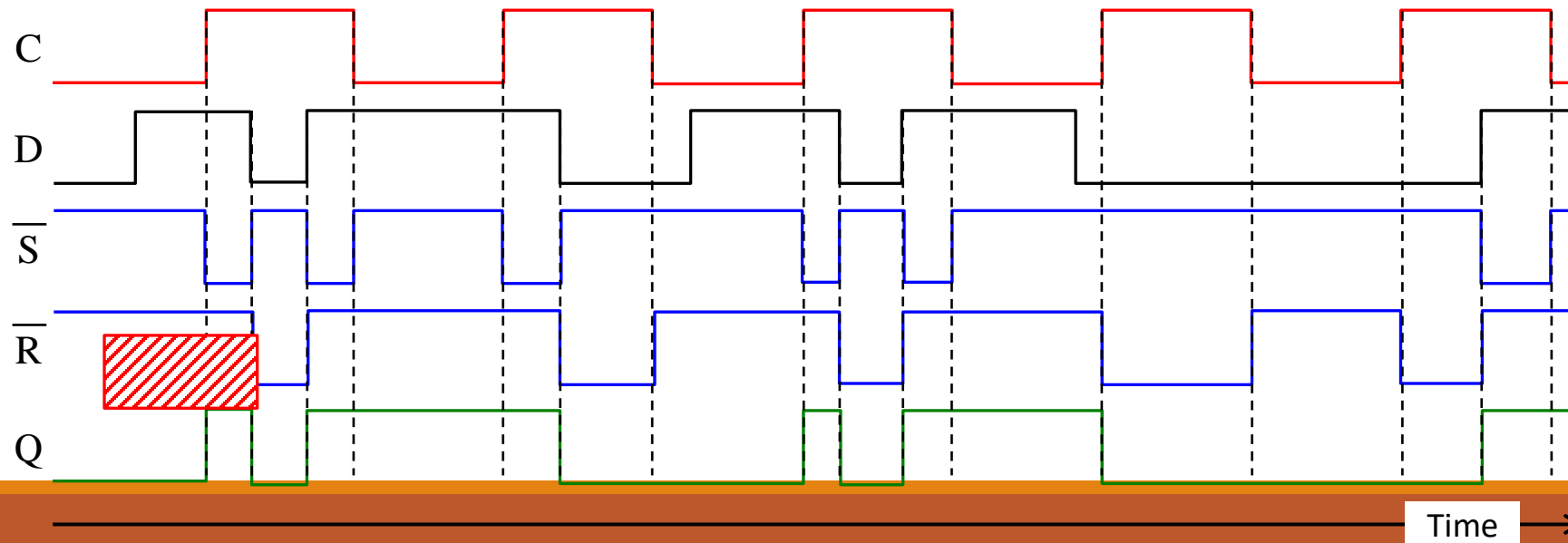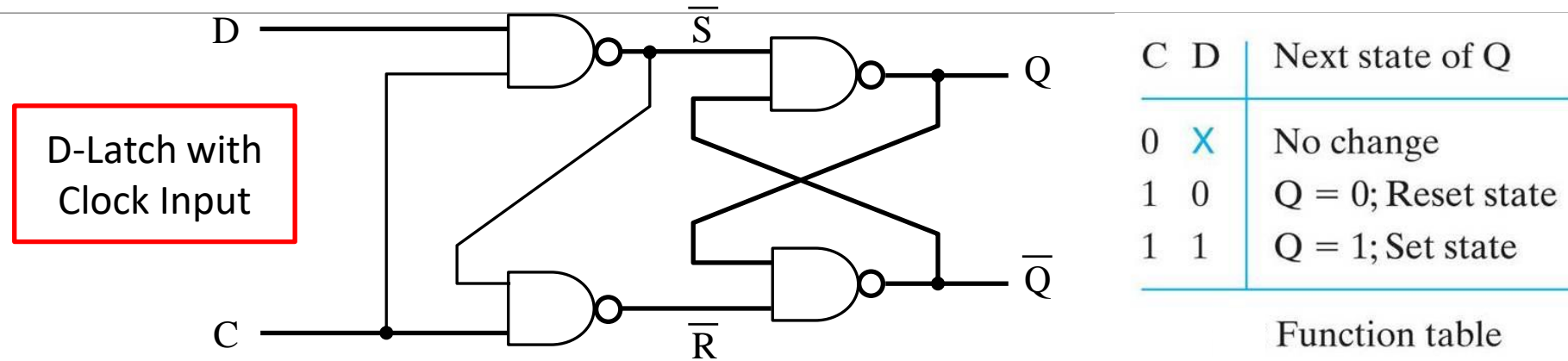

# Graphic Symbols for Latches

---

 

A bubble appears at the complemented output  $\overline{Q}$

Indicates that  $\overline{Q}$  is the complement of  $Q$

A bubble also appears at the inputs of an  $\overline{S} \overline{R}$  latch

Indicates that **logic-0** is used (not logic-1) to set (or reset) the latch (as in the NAND latch implementation)

# Problem with Latches

A latch is **level-sensitive** (sensitive to the level of the clock)


As long as the clock signal is **high** ...

Any change in the value of input  $D$  appears in the output  $Q$

Output  $Q$  keeps changing its value during a clock cycle

Final value of output  $Q$  is uncertain

 Due to this uncertainty,  
latches are NOT used as  
memory elements in  
synchronous circuits



# Flip-Flops

A **Flip-Flop** is a better memory element for synchronous circuits


Solves the problem of latches in synchronous sequential circuits

A **latch** is sensitive to the **level** of the clock

However, a **flip-flop** is sensitive to the **edge** of the clock

A flip-flop is called an **edge-triggered** memory element

 It changes its output value at the **edge** of the clock



# Edge-Triggered D Flip-Flop

Built using two latches in a **master-slave** configuration


A master latch (D-type) receives external inputs

A slave latch (SR-type) receives inputs from the master latch

Only one latch is enabled at any given time

When **Clk=0**, the master is enabled and the D input is latched (slave disabled)

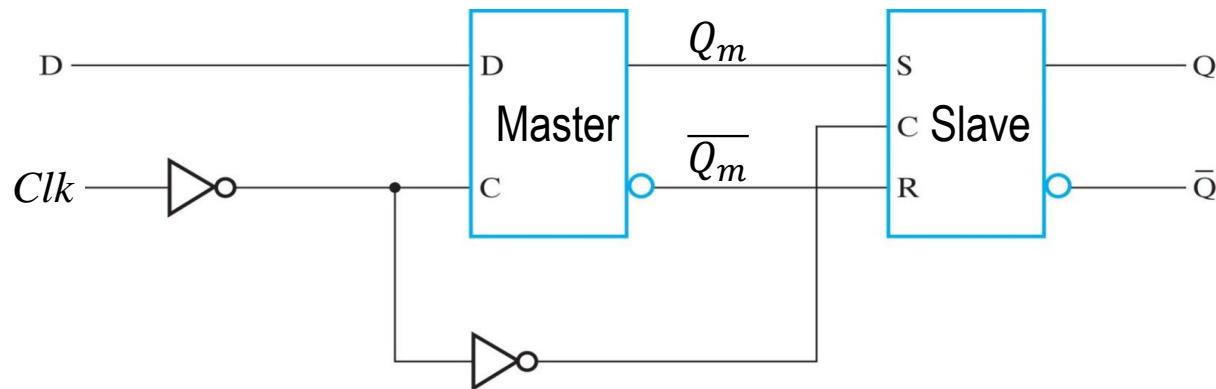When **Clk=1**, the slave is enabled to generate the outputs (master is disabled)



Outputs change  
when *Clk*  
changes **from 0**  
**to 1**

# Negative Edge-Triggered D Flip-Flop


Similar to positive edge-triggered flip-flop

The first inverter at the Master C input is removed

Only one latch is enabled at any given time

When **Clk=1**, the master is enabled and the D input is latched (slave disabled)

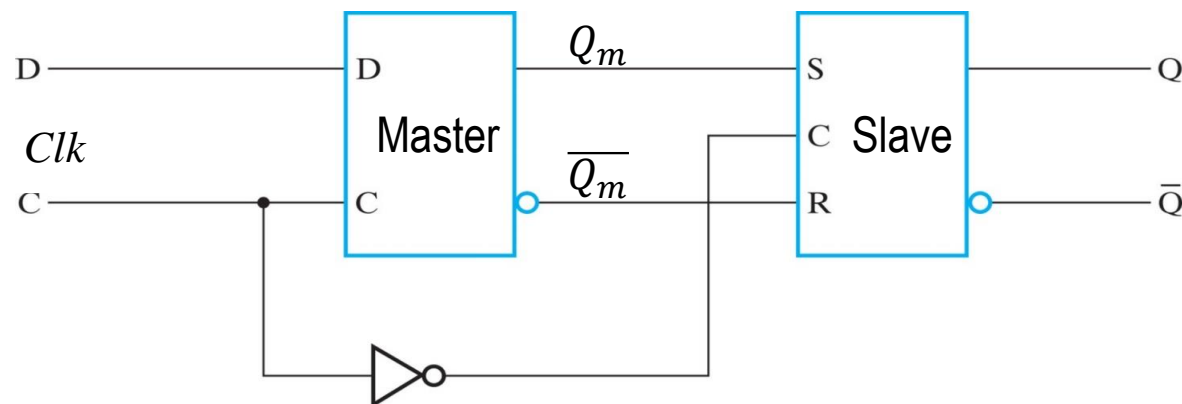When **Clk=0**, the slave is enabled to generate the outputs (master is disabled)



Outputs change  
when Clk  
changes **from 1**  
**to 0**




# D Flip-Flop Timing Diagram

The diagram shows the timing of a positive-edge D Flip-Flop

The master latch changes its output  $Q_m$  when the clock  $C$  is 0


The rising edge of the clock triggers the D Flip-Flop

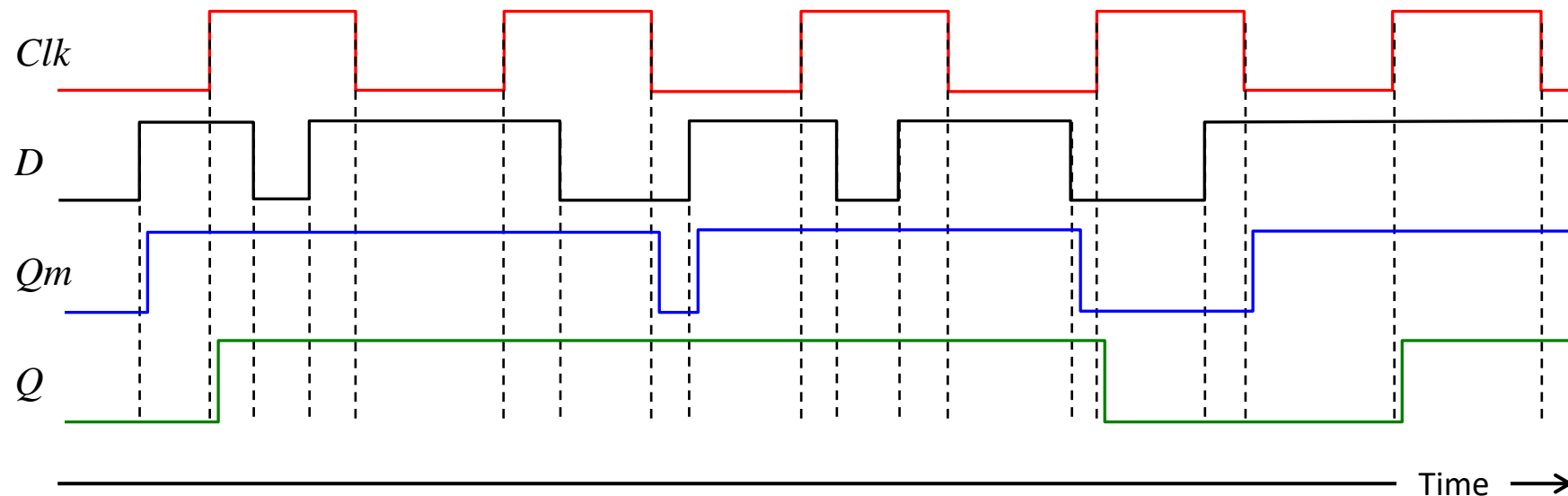Notice the slight delay in the output  $Q$  after the rising edge



# Graphic Symbols for Flip-Flops

---

 

A Flip-Flop has a similar symbol to a Latch

The difference is the arrowhead at the clock input

The arrowhead indicates sensitivity to the edge of the clock

A circle at the *Clk* input indicates negative edge-triggered FF


# Asynchronous Set and Reset

When Flip-Flops are powered, their initial state is **unknown**

Some flip-flops have an **asynchronous Set** and **Reset** inputs

Set forces  $Q$  to become **1**, independently of the clock

 Reset forces  $Q$  to become **0**, independently of the clock



Inputs				Outputs	
$\overline{Set}$	$\overline{Reset}$	$Data$	$Clk$	$Q$	$\overline{Q}$
0	1	X	X	1	0
1	0	X	X	0	1
1	1	0	↑	0	1
1	1	1	↑	1	0

Function Table

# JK Flip-Flop


The *D* Flip-Flop is the most commonly used type

The *JK* is another type of Flip-Flop with inputs: *J*, *K*, and *Clk*

When  $JK = 10 \rightarrow$  Set, When  $JK = 01 \rightarrow$  Reset

When  $JK = 00 \rightarrow$  No change, When  $JK = 11 \rightarrow$  Invert outputs

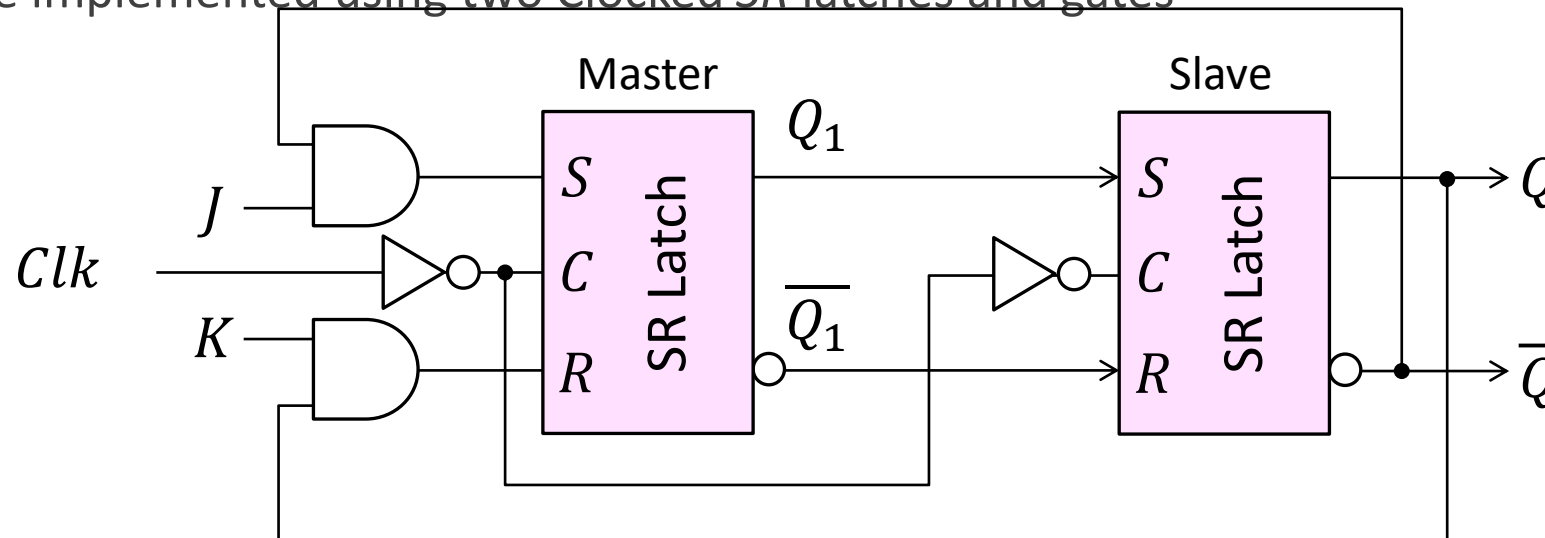*JK* can be implemented using two Clocked *SR* latches and gates




# T Flip-Flop

The  $T$  (Toggle) flip-flop has inputs:  $T$  and  $Clk$


When  $T = 0 \rightarrow$  No change, When  $T = 1 \rightarrow$  Invert outputs

The  $T$  flip-flop can be implemented using a  $JK$  flip-flop

 
It can also be implemented using a  $D$  flip-flop and a XOR gate



(a) From  $JK$  flip-flop

 

(b) From  $D$  flip-flop

 

(c) Graphic symbol

# Flip-Flop Characteristic Table

Defines the operation of a flip-flop in a tabular form

Next state is defined in terms of the current state and the inputs

$Q(t)$  refers to current state **before** the clock edge arrives

$Q(t + 1)$  refers to next state **after** the clock edge arrives

D Flip-Flop			JK Flip-Flop			T Flip-Flop		
$D$	$Q(t+1)$		$J$ $K$	$Q(t+1)$		$T$	$Q(t+1)$	
0	0	Reset	0 0	$Q(t)$	No change	0	$Q(t)$	No change
1	1	Set	0 1	0	Reset	1	$Q'(t)$	Complement
			1 0	1	Set			
			1 1	$Q'(t)$	Complement			

# Flip-Flop Characteristic Equation

The characteristic equation defines the operation of a flip-flop

For D Flip-Flop:  $Q(t + 1) = D$

For JK Flip-Flop:  $Q(t + 1) = J Q'(t) + K' Q(t)$

For T Flip-Flop:  $Q(t + 1) = T \oplus Q(t)$

Clearly, the D Flip-Flop is the simplest among the three

D Flip-Flop		
$D$	$Q(t+1)$	
0	0	Reset
1	1	Set

JK Flip-Flop			
$J$	$K$	$Q(t+1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

T Flip-Flop		
$T$	$Q(t+1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

# Summary

---

In a sequential circuit there is internal memory

- Output is a function of current inputs and present state
- The stored memory value defines the present state
- Similarly, the next state depends on current inputs and present state

Two types of sequential circuits:

- Synchronous sequential circuits are clocked (easier to implement)
- Asynchronous sequential circuits are not clocked

Two types of Memory elements: Latches and Flip-Flops

Latches are level-sensitive, flip-flops are edge-triggered

Flip-flops are better memory elements for synchronous circuits

A flip-flop is described using a characteristic table and equation